

Computer System Architecture

COMP201Th

Lecture: 9

Decoders

Discrete quantities of information are represented in digital computers with binary codes. A binary code of n bits is capable of representing upto 2^n distinct elements of the coded information.


- **Decoders:**

- A decoder is a combinational circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs.
- A decoder has n inputs and m outputs and is also referred to as $n \times m$ decoder.
- Decoding is essential in applications like memory address decoding and 7 segment display.



- **2 to 4 Decoder:**

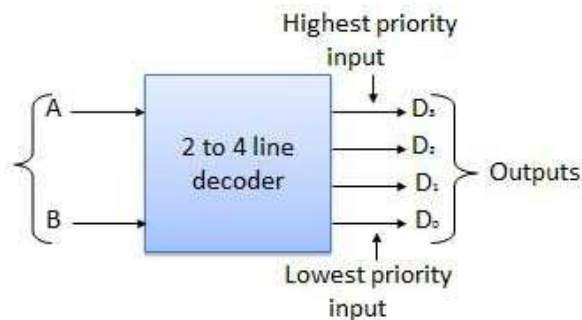
- 2 to 4 decoder has two inputs and 4 outputs.




- Decoder have two inputs namely A, B and four outputs denoted by D_0, D_1, D_2, D_3 . The truth table for 2 to 4 decoder is:

Inputs		Output			
A	B	D0	D1	D2	D3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 - Logic circuit for 2 to 4 decoder is as below:



 
- Commercial decoders include one or more enable inputs to control the operation of the circuit. The decoder is enabled when E is equal to 1 and disabled when E is equal to 0.



- **Enable inputs are a convenient feature for interconnecting two or more circuits for the purpose of expanding the digital component into a similar function but with more inputs and outputs.**

- **NAND Gate Decoder:**

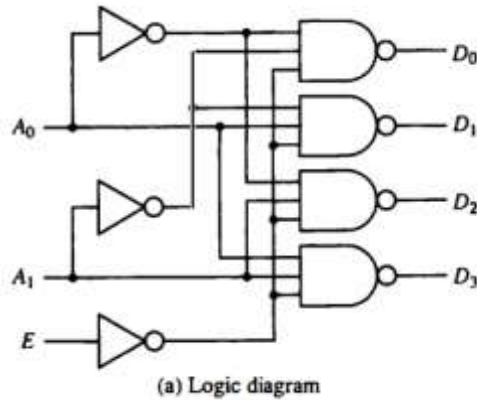- Its more economical to use NAND instead of AND gates as they are easy to fabricate.



E	A_1	A_0	D_0	D_1	D_2	D_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1


(b) Truth table

Fig. 2 to 4 Decoder using NAND gates.


- **In general a decoder may operate with complemented or uncomplemented outputs.**

- **Decoder Expansion:**

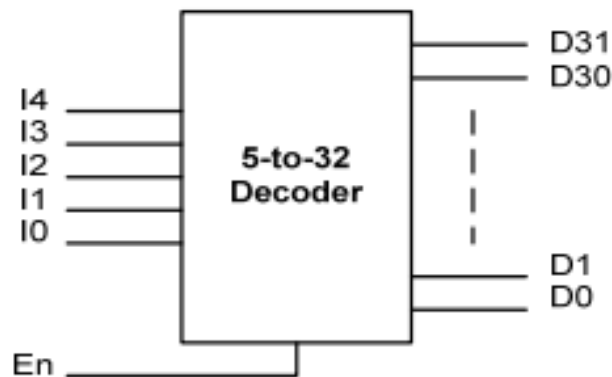- It is possible to combine two or more decoders with enable inputs to form a larger decoder.
- e.g. Construct a 5 to 32 line decoder using 3 to 8 line decoder with Enable and 2 to 4 line decoder.



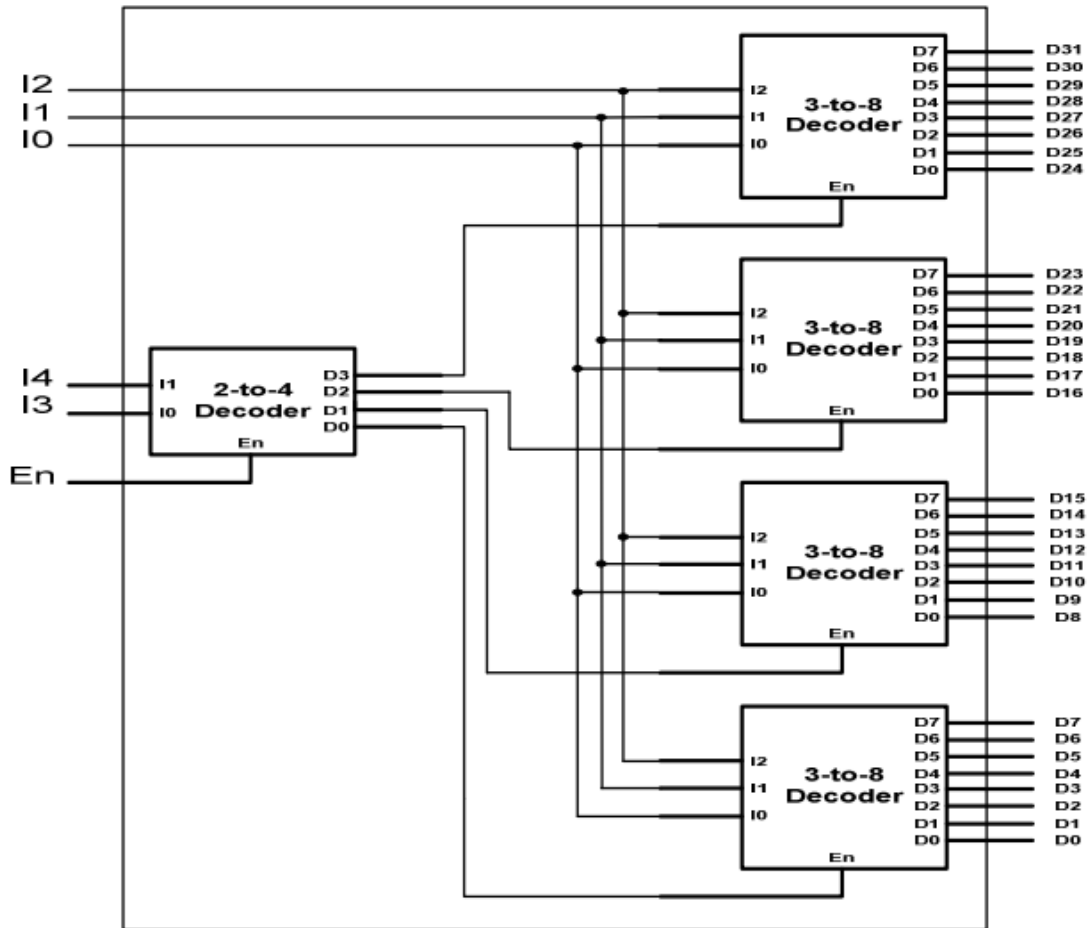Here output is 32 so we can say that we need four 3-to-8 decoder and to select (i.e. to Enable them) we need one 2-to-4 decoder.



- **Any combinational circuit with n inputs and m outputs can be implemented with an n to 2^n line decoder and m OR gates.**